



5. a) Design full subtractor circuit using two half subtractor & one OR gate. Also draw the logic circuit & give its truth table. 6
- b) Implement the following function using 8:1 MUX. Use W, X, Y as select lines. 7
- $$F(W, X, Y, Z) = \prod M(0, 1, 4, 6, 9, 10, 11, 15)$$

**OR**

6. a) Design 3 bit binary to grey code converter. 7
- b) Design & implement 3 input priority encoder. 6
7. a) Convert the following 8
- 1) SR flip flop to JK flip flop
  - 2) JK flip flop to T flip flop
- b) What is race around condition in JK flip flop? How it is eliminated by using JK-Master slave flip-flop. 6

**OR**

8. a) Design lock free counter to count in following sequence (Use T Flip Flop) 8
- $$\begin{array}{c} 1 \\ \uparrow \end{array} \rightarrow 3 \rightarrow \begin{array}{c} 4 \\ \downarrow \end{array}$$
- $$6 \leftarrow 7 \leftarrow 5$$
- b) Draw the logic diagram of JK flip-flop using NAND gate & explain its working. 6
9. a) Define addressing mode. Explain different addressing mode of 8085 microprocessor with one example each. 7
- b) Explain the following instruction 6
- 1) XTHL
  - 2) DAA
  - 3) DAD R<sub>p</sub>
  - 4) LDAX B

**OR**

10. a) Draw & explain the architecture of 8085 microprocessor in detail. 8
- b) Draw & Explain the flag register of 8085 microprocessor. 5
11. a) Draw & explain interrupt structure of 8085 microprocessor in detail. 7
- b) Draw & explain timing diagram of instruction MVI A, 22H. 6

**OR**

12. a) Write an assembly language program to add 10 bytes of data. Data is present from 8000H & onwards memory location. Store answer in B register. 6
- b) Draw & explain RIM & SIM instruction of 8085 microprocessor. 7

\*\*\*\*\*